### **CS2310: Foundations of Computer System Design Lab**

## **August-November 2021 Semester**

### **Assignment 2**

Date: 24<sup>th</sup> August, 2021

Deadline for Submission: 11.59PM on 30<sup>th</sup> August, 2021

The test data details are indicated for each question

1. **2-bit 4-to-1 multiplexer:** For each of the 4 sources, all the 4 combinations of 2-bit data

### 2. **2-bit 4-to-1** priority multiplexer:

- a) Only one request input to the priority encoder is active. For that device, all the 4 combinations of 2-bit data.
- b) At least 2 request inputs to the priority encoder are active. 4 different combinations of the request inputs, and one combination of 2-bit data for combination of request inputs.
- 3. **2-bit 1-to-8 demultiplexer:** For each of the 8 destination devices, one combination of 2-bit input data

# 4. 8-bit comparator:

- a) 2 sets of input operands that are the same.
- b) 2 sets of input operands that are different.
- 5. **8-bit parity generator and parity checker:** 4 different combinations of 8-bit data. For each combination, 2 cases of 1-bit error in a data bit or the parity bit, and 1 case of no error either in data bits or parity bit.