

CS2310: Foundations of Computer System Design Lab
August-November 2021 Semester
Assignment 5

Date: 21st September, 2021

Deadline for Submission: 11.59PM on 27th September, 2021

Design of an 8-bit ALU with specifications given separately.

Test cases for logical operations

- 1 pair of operands with X not equal to Y, for NOP
- 1 pair of operands with X equal to Y, for NOP
- 1 pair of operands for each logical operation (AND, OR, XOR)

Test cases for arithmetic operations:

1 pair of operands that does not result in an overflow for each of the following arithmetic operations:

- Unsigned addition
- Unsigned subtraction with $X > Y$
- Signed addition
- Signed subtraction
- Unsigned multiplication
- Signed multiplication

1 pair of operands that results in an overflow for each of the following arithmetic operations:

- Unsigned addition
- Signed addition
- Signed subtraction
- Unsigned multiplication
- Signed multiplication